 


# LAB 1 – Raja Aadhithan

Design - Full adder using Half adder:


Wave:



Output:

```
# Input a=0, b=0, c=0, Output sum =0, carry=0
# Input a=0, b=0, c=1, Output sum =1, carry=0
# Input a=0, b=1, c=0, Output sum =1, carry=0
# Input a=0, b=1, c=1, Output sum =0, carry=1
# Input a=1, b=0, c=0, Output sum =1, carry=0
# Input a=1, b=0, c=1, Output sum =0, carry=1
# Input a=1, b=1, c=0, Output sum =0, carry=1
# Input a=1, b=1, c=1, Output sum =1, carry=1
```

RTL:

 

## Exercises:

Design : Ripple adder


Wave:

/ripple_adder_tb/a	1001	0000	0001	0010	0011	0100	0101	0110	0111	1000	1001
/ripple_adder_tb/b	1001	0000	0001	0010	0011	0100	0101	0110	0111	1000	1001
/ripple_adder_tb/c	0										
/ripple_adder_tb/s	0010	0001	0010	0101	0110	1001	1010	1101	1110	0001	0010
/ripple_adder_tb/cy	St1										
/ripple_adder_tb/i	9	0	1	2	3	4	5	6	7	8	9

Output:


```
VSIM 28> run -all
# Input a=0000, b=0000, c=1, Output sum =0001, carry=0
# Input a=0001, b=0001, c=0, Output sum =0010, carry=0
# Input a=0010, b=0010, c=1, Output sum =0101, carry=0
# Input a=0011, b=0011, c=0, Output sum =0110, carry=0
# Input a=0100, b=0100, c=1, Output sum =1001, carry=0
# Input a=0101, b=0101, c=0, Output sum =1010, carry=0
# Input a=0110, b=0110, c=1, Output sum =1101, carry=0
# Input a=0111, b=0111, c=0, Output sum =1110, carry=0
# Input a=1000, b=1000, c=1, Output sum =0001, carry=1
# Input a=1001, b=1001, c=0, Output sum =0010, carry=1
# ** Note: $finish      : C:/Users/Aadhithan/Documents/Verilog_labs/lab1/sim/ripple_ad
der_tb.v(26)
#   Time: 100 ps  Iteration: 0  Instance: /ripple_adder_tb
```

RTL:

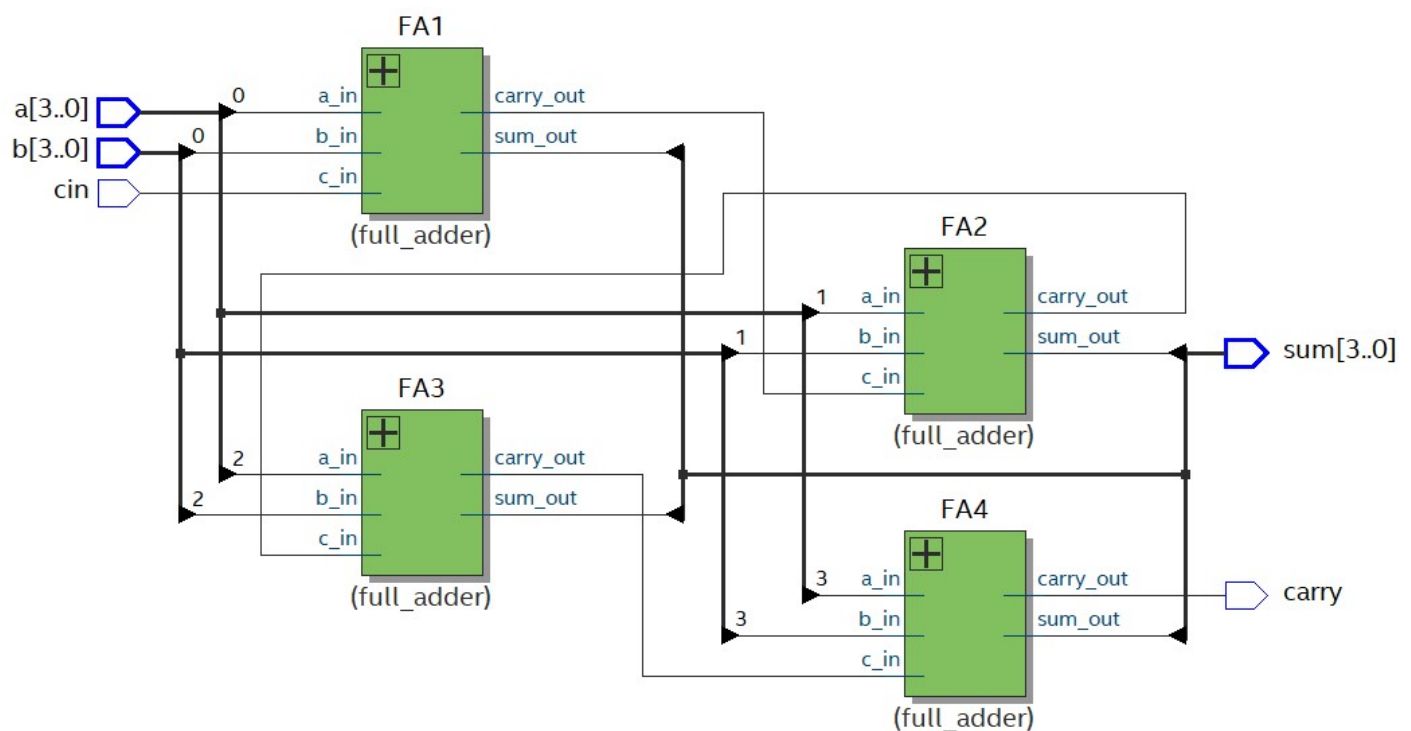

## Design : 4:1 mux using 2:1 mux

Wave:

 

Output:

```
VSIM 34> run -all
# @time: 0- selct is 00 nad input is 0,0,0,0 for output is 0
# @time: 10- selct is 00 nad input is 0,0,0,1 for output is 0
# @time: 20- selct is 00 nad input is 0,0,1,0 for output is 0
# @time: 30- selct is 00 nad input is 0,0,1,1 for output is 0
# @time: 40- selct is 00 nad input is 0,1,0,0 for output is 0
# @time: 50- selct is 00 nad input is 0,1,0,1 for output is 0
# @time: 60- selct is 00 nad input is 0,1,1,0 for output is 0
# @time: 70- selct is 00 nad input is 0,1,1,1 for output is 0
# @time: 80- selct is 00 nad input is 1,0,0,0 for output is 1
# @time: 90- selct is 00 nad input is 1,0,0,1 for output is 1
# @time:100- selct is 00 nad input is 1,0,1,0 for output is 1
# @time:110- selct is 00 nad input is 1,0,1,1 for output is 1
# @time:120- selct is 00 nad input is 1,1,0,0 for output is 1
# @time:130- selct is 00 nad input is 1,1,0,1 for output is 1
# @time:140- selct is 00 nad input is 1,1,1,0 for output is 1
# @time:150- selct is 00 nad input is 1,1,1,1 for output is 1
# @time:160- selct is 01 nad input is 0,0,0,0 for output is 0
# @time:170- selct is 01 nad input is 0,0,0,1 for output is 0
# @time:180- selct is 01 nad input is 0,0,1,0 for output is 0
# @time:190- selct is 01 nad input is 0,0,1,1 for output is 0
# @time:200- selct is 01 nad input is 0,1,0,0 for output is 1
# @time:210- selct is 01 nad input is 0,1,0,1 for output is 1
# @time:220- selct is 01 nad input is 0,1,1,0 for output is 1
# @time:230- selct is 01 nad input is 0,1,1,1 for output is 1
# @time:240- selct is 01 nad input is 1,0,0,0 for output is 0
# @time:250- selct is 01 nad input is 1,0,0,1 for output is 0
# @time:260- selct is 01 nad input is 1,0,1,0 for output is 0
# @time:270- selct is 01 nad input is 1,0,1,1 for output is 0
# @time:280- selct is 01 nad input is 1,1,0,0 for output is 1
# @time:290- selct is 01 nad input is 1,1,0,1 for output is 1
# @time:300- selct is 01 nad input is 1,1,1,0 for output is 1
# @time:310- selct is 01 nad input is 1,1,1,1 for output is 1
# @time:320- selct is 10 nad input is 0,0,0,0 for output is 0
# @time:330- selct is 10 nad input is 0,0,0,1 for output is 0
```




```

# @time:330- selstc is 10 nad input is 0,0,0,1 for output is 0
# @time:340- selstc is 10 nad input is 0,0,1,0 for output is 1
# @time:350- selstc is 10 nad input is 0,0,1,1 for output is 1
# @time:360- selstc is 10 nad input is 0,1,0,0 for output is 0
# @time:370- selstc is 10 nad input is 0,1,0,1 for output is 0
# @time:380- selstc is 10 nad input is 0,1,1,0 for output is 1
# @time:390- selstc is 10 nad input is 0,1,1,1 for output is 1
# @time:400- selstc is 10 nad input is 1,0,0,0 for output is 0
# @time:410- selstc is 10 nad input is 1,0,0,1 for output is 0
# @time:420- selstc is 10 nad input is 1,0,1,0 for output is 1
# @time:430- selstc is 10 nad input is 1,0,1,1 for output is 1
# @time:440- selstc is 10 nad input is 1,1,0,0 for output is 0
# @time:450- selstc is 10 nad input is 1,1,0,1 for output is 0
# @time:460- selstc is 10 nad input is 1,1,1,0 for output is 1
# @time:470- selstc is 10 nad input is 1,1,1,1 for output is 1
# @time:480- selstc is 11 nad input is 0,0,0,0 for output is 0
# @time:490- selstc is 11 nad input is 0,0,0,1 for output is 1
# @time:500- selstc is 11 nad input is 0,0,1,0 for output is 0
# @time:510- selstc is 11 nad input is 0,0,1,1 for output is 1
# @time:520- selstc is 11 nad input is 0,1,0,0 for output is 0
# @time:530- selstc is 11 nad input is 0,1,0,1 for output is 1
# @time:540- selstc is 11 nad input is 0,1,1,0 for output is 0
# @time:550- selstc is 11 nad input is 0,1,1,1 for output is 1
# @time:560- selstc is 11 nad input is 1,0,0,0 for output is 0
# @time:570- selstc is 11 nad input is 1,0,0,1 for output is 1
# @time:580- selstc is 11 nad input is 1,0,1,0 for output is 0
# @time:590- selstc is 11 nad input is 1,0,1,1 for output is 1
# @time:600- selstc is 11 nad input is 1,1,0,0 for output is 0
# @time:610- selstc is 11 nad input is 1,1,0,1 for output is 1
# @time:620- selstc is 11 nad input is 1,1,1,0 for output is 0
# @time:630- selstc is 11 nad input is 1,1,1,1 for output is 1
# ** Note: $finish      : C:/Users/Aadhithan/Documents/Verilog_labs/lab1/4_2_mux/muv4_
tb.v(16)
#   Time: 1 ns  Iteration: 0  Instance: /mux4_tb
# 1

```


RTL:

 

## Assignment:


Design: RTL for full adder.

RTL:

 

Design: 2x4 decoder.

 


RTL:



Design: 8x3 priority encoder.

Wave:


Msgs									
+ /encoder_tb/x	000...	00000001	00000000	00000010	00000100	00001000	00000110		
+ /encoder_tb/y	011	000	001	010	011	010			
+ /encoder_tb/i	8	0	1	2	3				

		Msgs																			
	/encoder_tb/x	000...	00001000	00000110		00010000		00001000		00100000		00001010		01000000		00001100		10000000		00001110	
	/encoder_tb/y	011	011	010		100		011		101		011		110		011		111		011	
	/encoder_tb/j	8	3			4				5				6				7			

Output:


```
VSIM 38> run -all
# @ time: 0ps the input is 00000001 output is 000
# @ time: 10ps the input is 00000000 output is 000
# @ time: 20ps the input is 00000010 output is 001
# @ time: 40ps the input is 00000100 output is 010
# @ time: 60ps the input is 00001000 output is 011
# @ time: 70ps the input is 00000110 output is 010
# @ time: 80ps the input is 00010000 output is 100
# @ time: 90ps the input is 00001000 output is 011
# @ time: 100ps the input is 00100000 output is 101
# @ time: 110ps the input is 00001010 output is 011
# @ time: 120ps the input is 01000000 output is 110
# @ time: 130ps the input is 00001100 output is 011
# @ time: 140ps the input is 10000000 output is 111
# @ time: 150ps the input is 00001110 output is 011
# ** Note: $finish : C:/Users/Aadhithan/Documents/Verilog_labs/lab1/encoder/encoder_tb.v(14)
# Time: 160 ps Iteration: 0 Instance: /encoder tb
```

RTL:

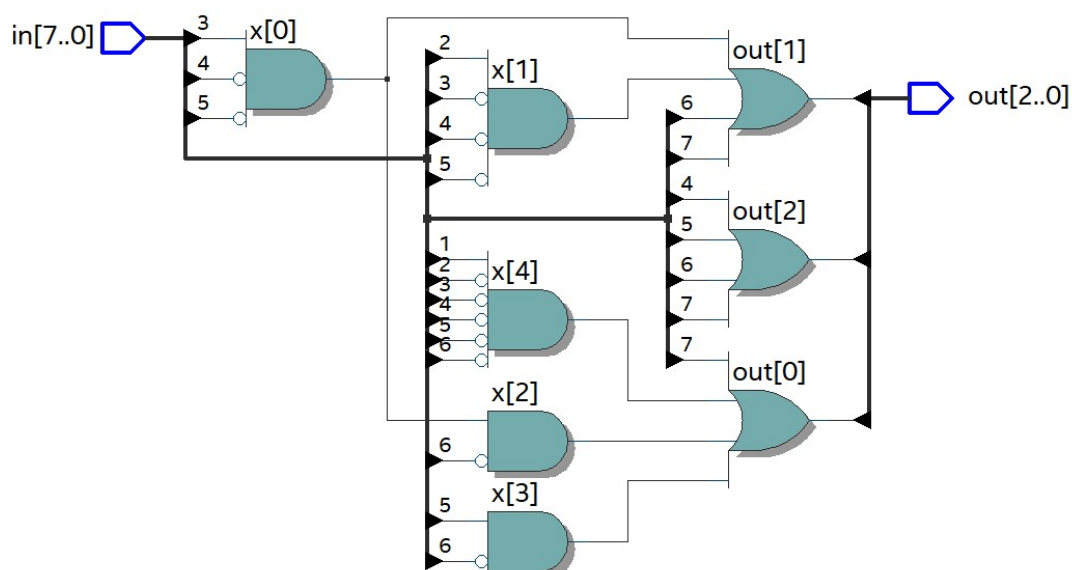


Design: 4x1 mux.

Wave:

 


RTL:

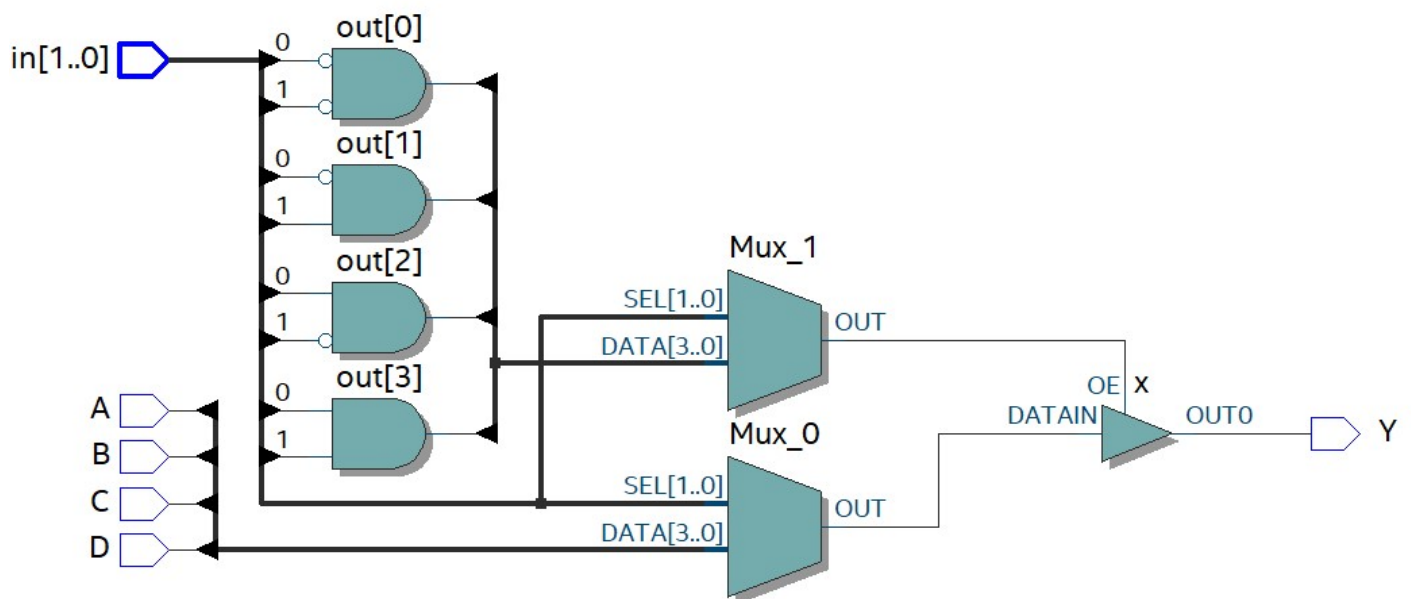

Design: Bidirectional buffer

Wave:

 



## Output:

```
VSIM 49> run -all
# @time = 0: The value of a is 0 and b is 0
# enable is 0
# output ar is 0 and br is z
# @time = 10: The value of a is 0 and b is 0
# enable is 1
# output ar is z and br is 0
# @time = 20: The value of a is 0 and b is 1
# enable is 0
# output ar is 1 and br is z
# @time = 30: The value of a is 0 and b is 1
# enable is 1
# output ar is z and br is 0
# @time = 40: The value of a is 1 and b is 0
# enable is 0
# output ar is 0 and br is z
# @time = 50: The value of a is 1 and b is 0
# enable is 1
# output ar is z and br is 1
# @time = 60: The value of a is 1 and b is 1
# enable is 0
# output ar is 1 and br is z
# @time = 70: The value of a is 1 and b is 1
# enable is 1
# output ar is z and br is 1
# @time = 80: The value of a is 0 and b is 0
# enable is 0
# output ar is 0 and br is z
# @time = 90: The value of a is 0 and b is 0
# enable is 1
# output ar is z and br is 0
# @time = 100: The value of a is 0 and b is 1
# enable is 0
# output ar is 1 and br is z
# @time = 110: The value of a is 0 and b is 1
# enable is 1
# output ar is z and br is 0
# @time = 120: The value of a is 1 and b is 0
# enable is 0
# output ar is 0 and br is z
# @time = 130: The value of a is 1 and b is 0
# enable is 1
# output ar is z and br is 1
# @time = 140: The value of a is 1 and b is 1
# enable is 0
# output ar is 1 and br is z
# @time = 150: The value of a is 1 and b is 1
# enable is 1
# output ar is z and br is 1
```

## RTL:

