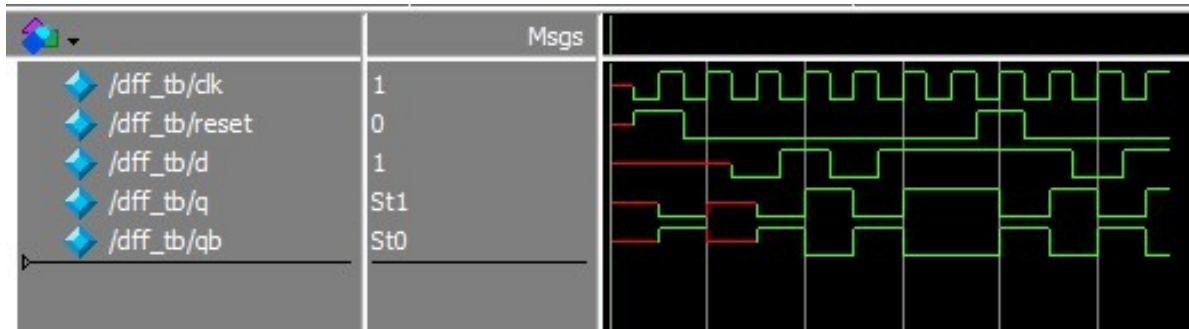


LAB 4 – Raja Aadhithan

Design – D Flip Flop:


Wave:



Output:

```
VSIM 17> run -all
# @time: 0ps the input: x, reset:x, output is x,x
# @time: 5ps the input: x, reset:1, output is x,x
# @time: 10ps the input: x, reset:1, output is 0,1
# @time: 15ps the input: x, reset:0, output is 0,1
# @time: 20ps the input: x, reset:0, output is x,x
# @time: 25ps the input: 0, reset:0, output is x,x
# @time: 30ps the input: 0, reset:0, output is 0,1
# @time: 35ps the input: 1, reset:0, output is 0,1
# @time: 40ps the input: 1, reset:0, output is 1,0
# @time: 45ps the input: 0, reset:0, output is 1,0
# @time: 50ps the input: 0, reset:0, output is 0,1
# @time: 55ps the input: 1, reset:0, output is 0,1
# @time: 60ps the input: 1, reset:0, output is 1,0
# @time: 75ps the input: 1, reset:1, output is 1,0
# @time: 80ps the input: 1, reset:1, output is 0,1
# @time: 85ps the input: 1, reset:0, output is 0,1
# @time: 90ps the input: 1, reset:0, output is 1,0
# @time: 95ps the input: 0, reset:0, output is 1,0
# @time: 100ps the input: 0, reset:0, output is 0,1
# @time: 105ps the input: 1, reset:0, output is 0,1
# @time: 110ps the input: 1, reset:0, output is 1,0
# ** Note: $finish : C:/Users/Aadhithan/Documents
# Time: 115 ps Iteration: 0 Instance: /dff_tb
```


RTL:

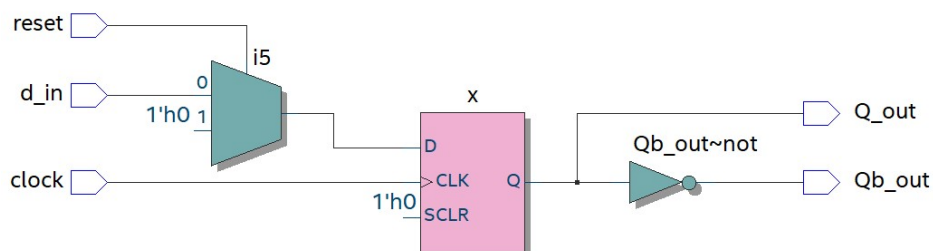

Exercises:

Design : SR latch:


Wave:

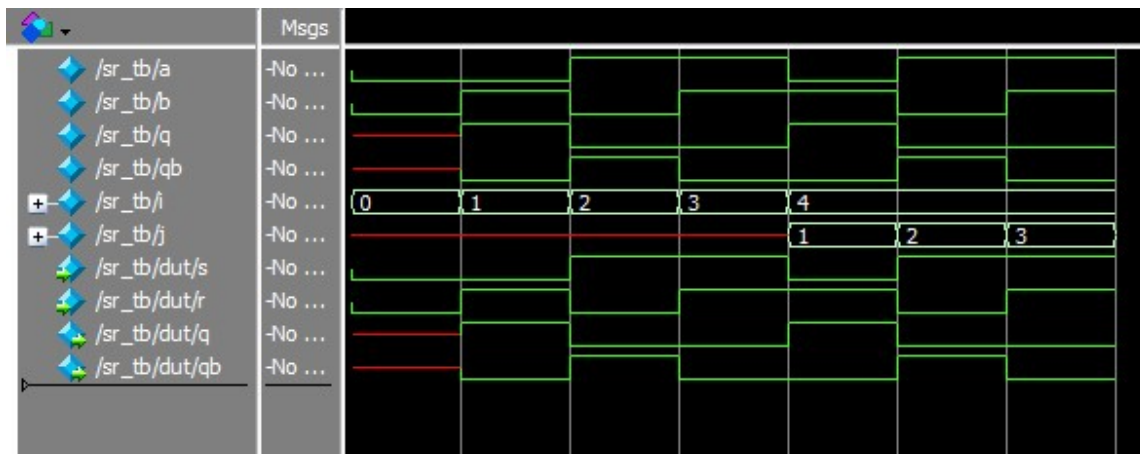

Output:


```
VSIM 24> run -all
# @time 0 input is 0,0 - output is x,x
# @time 10 input is 0,1 - output is 1,0
# @time 20 input is 1,0 - output is 0,1
# @time 30 input is 1,1 - output is 0,0
# @time 40 input is 0,1 - output is 1,0
# @time 50 input is 1,0 - output is 0,1
# @time 60 input is 1,1 - output is 0,0
# ** Note: $finish : C:/Users/Aadhithar
# Time: 70 ps Iteration: 0 Instance:
1
```

RTL:

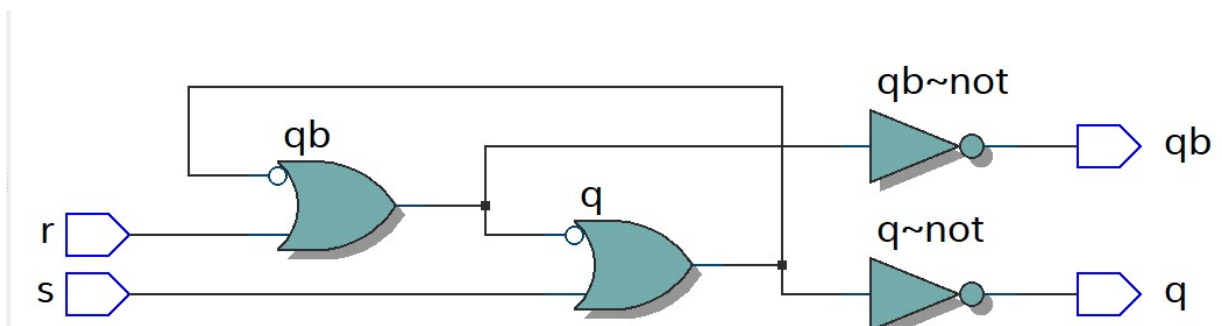

Design: JK Flip Flop:


Wave:

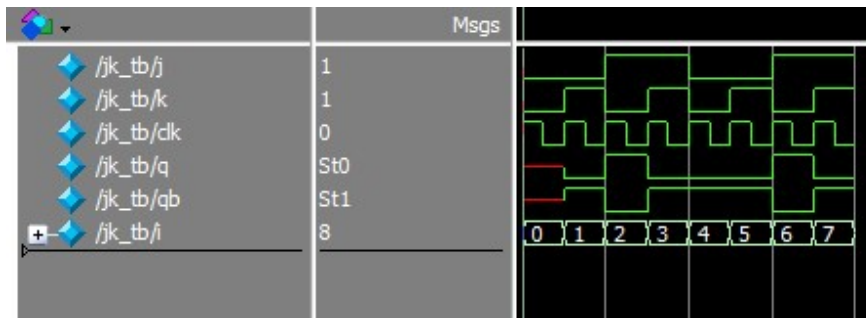

Output:


```
VSIM 28> run -all
# @time : 0: j is 0, k is 0, output is x-x
# @time : 10: j is 0, k is 1, output is 0-1
# @time : 20: j is 1, k is 0, output is 1-0
# @time : 30: j is 1, k is 1, output is 0-1
# @time : 40: j is 0, k is 0, output is 0-1
# @time : 50: j is 0, k is 1, output is 0-1
# @time : 60: j is 1, k is 0, output is 1-0
# @time : 70: j is 1, k is 1, output is 0-1
# ** Note: $finish : C:/Users/Aadhithan/Docume
b.v(17)
# Time: 80 ps Iteration: 0 Instance: /jk_tb
```

RTL:

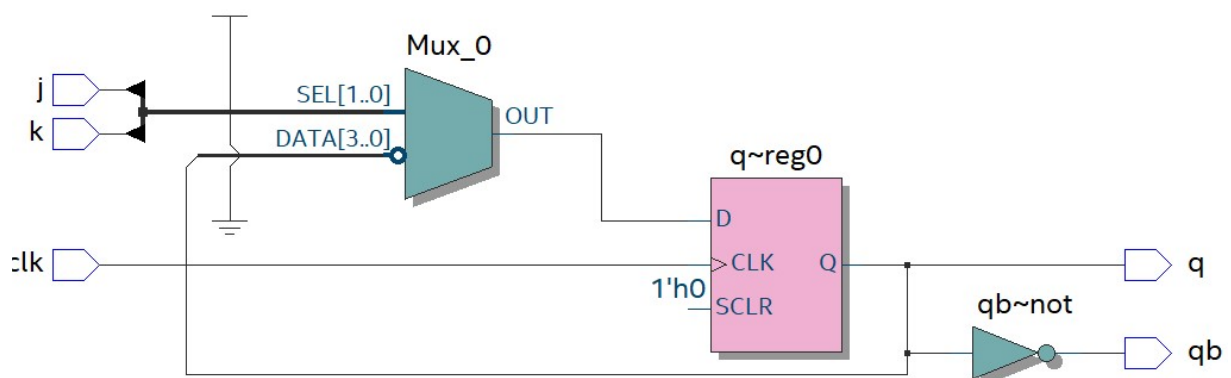

Design : T Flip Flop:


Wave:

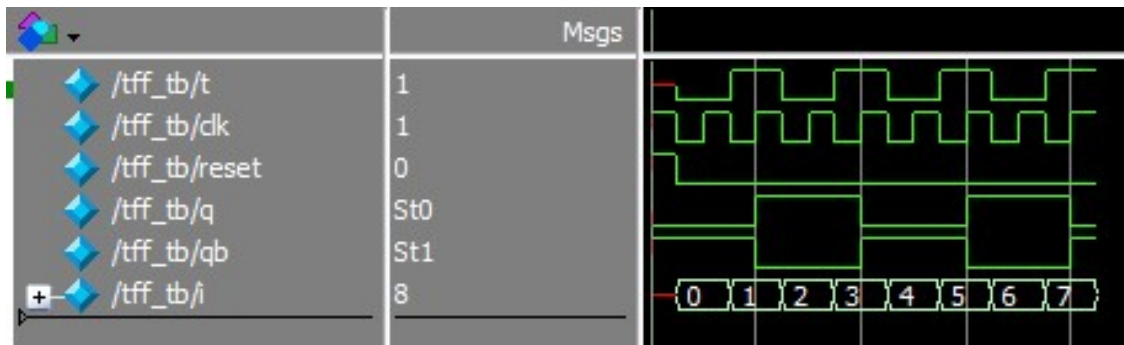

Output:

```
VSIM 32> run -all
# @time = 0: T is x and outputs are 0 - 1
# @time = 5: T is 0 and outputs are 0 - 1
# @time = 15: T is 1 and outputs are 0 - 1
# @time = 20: T is 1 and outputs are 1 - 0
# @time = 25: T is 0 and outputs are 1 - 0
# @time = 35: T is 1 and outputs are 1 - 0
# @time = 40: T is 1 and outputs are 0 - 1
# @time = 45: T is 0 and outputs are 0 - 1
# @time = 55: T is 1 and outputs are 0 - 1
# @time = 60: T is 1 and outputs are 1 - 0
# @time = 65: T is 0 and outputs are 1 - 0
# @time = 75: T is 1 and outputs are 1 - 0
# @time = 80: T is 1 and outputs are 0 - 1
# ** Note: $finish : C:/Users/Aadhithan/Docume
_tb.v(20)
# Time: 85 ps Iteration: 0 Instance: /tff_tb
```


RTL:

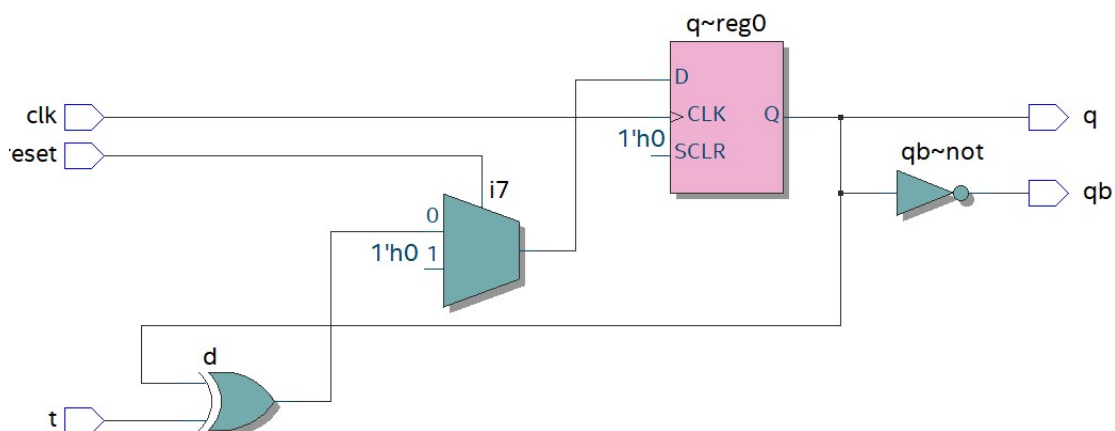

Design: 4 bit synchronous up counter:

Wave:


Zoomed out version:

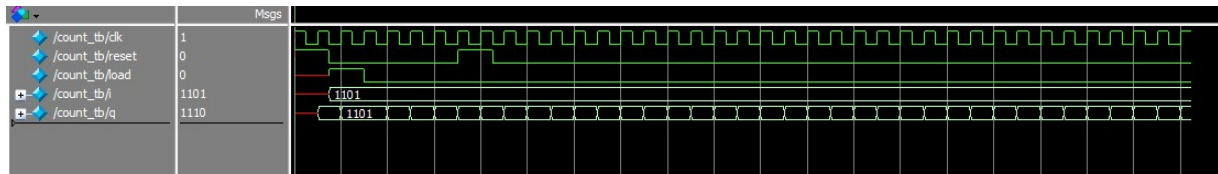

Output:


```
VSIM 36> run -all
# @time : 0 - for load = x output is xxxx
# @time : 10 - for load = x output is 0000
# @time : 15 - for load = 1 output is 0000
# @time : 20 - for load = 1 output is 1101
# @time : 30 - for load = 0 output is 1101
# @time : 40 - for load = 0 output is 1110
# @time : 50 - for load = 0 output is 1111
# @time : 60 - for load = 0 output is 0000
# @time : 70 - for load = 0 output is 0001
# @time : 80 - for load = 0 output is 0000
# @time : 90 - for load = 0 output is 0001
# @time : 100 - for load = 0 output is 0010
# @time : 110 - for load = 0 output is 0011
# @time : 120 - for load = 0 output is 0100
# @time : 130 - for load = 0 output is 0101
# @time : 140 - for load = 0 output is 0110
# @time : 150 - for load = 0 output is 0111
# @time : 160 - for load = 0 output is 1000
# @time : 170 - for load = 0 output is 1001
# @time : 180 - for load = 0 output is 1010
# @time : 190 - for load = 0 output is 1011
# @time : 200 - for load = 0 output is 1100
# @time : 210 - for load = 0 output is 1101
# @time : 220 - for load = 0 output is 1110
# @time : 230 - for load = 0 output is 1111
# @time : 240 - for load = 0 output is 0000
# @time : 250 - for load = 0 output is 0001
# @time : 260 - for load = 0 output is 0010
# @time : 270 - for load = 0 output is 0011
# @time : 280 - for load = 0 output is 0100
# @time : 290 - for load = 0 output is 0101
# @time : 300 - for load = 0 output is 0110
# @time : 310 - for load = 0 output is 0111
# @time : 320 - for load = 0 output is 1000
# @time : 330 - for load = 0 output is 1001
# @time : 340 - for load = 0 output is 1010
# @time : 350 - for load = 0 output is 1011
# @time : 360 - for load = 0 output is 1100
# @time : 370 - for load = 0 output is 1101
# @time : 380 - for load = 0 output is 1110
# ** Note: $finish : C:/Users/Aadhithan/Documents/
/count_tb.v(24)
# Time: 385 ps Iteration: 0 Instance: /count_tb
```


RTL:

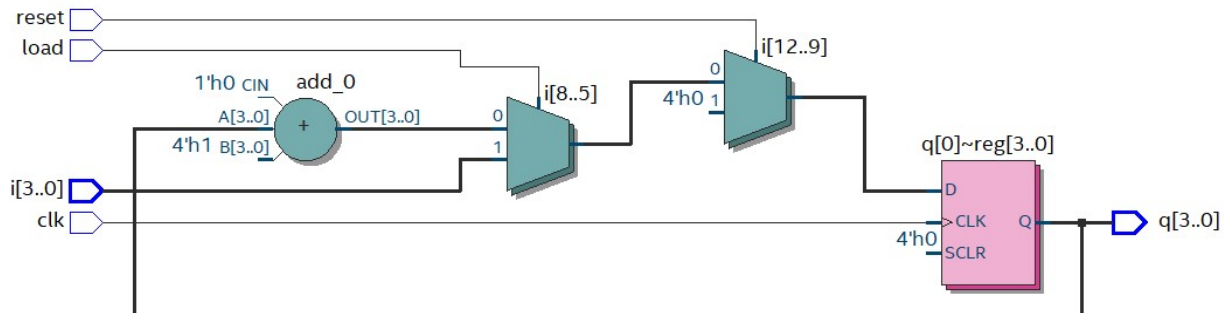

Design: Mod 12 counter;

Wave:

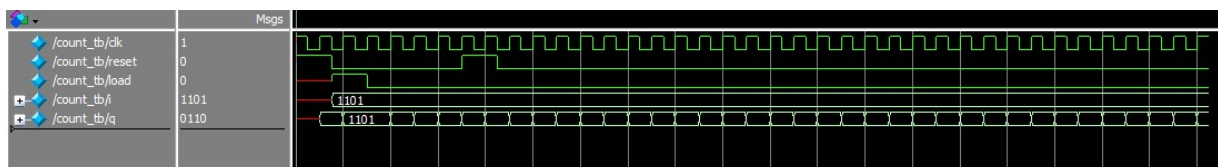


Output:

```

VSIM 40> run -all
# @time : 0 - for load = x output is xxxxx
# @time : 10 - for load = x output is 0000
# @time : 15 - for load = 1 output is 0000
# @time : 20 - for load = 1 output is 1101
# @time : 30 - for load = 0 output is 1101
# @time : 40 - for load = 0 output is 1110
# @time : 50 - for load = 0 output is 1111
# @time : 60 - for load = 0 output is 0000
# @time : 70 - for load = 0 output is 0001
# @time : 80 - for load = 0 output is 0000
# @time : 90 - for load = 0 output is 0001
# @time : 100 - for load = 0 output is 0010
# @time : 110 - for load = 0 output is 0011
# @time : 120 - for load = 0 output is 0100
# @time : 130 - for load = 0 output is 0101
# @time : 140 - for load = 0 output is 0110
# @time : 150 - for load = 0 output is 0111
# @time : 160 - for load = 0 output is 1000
# @time : 170 - for load = 0 output is 1001
# @time : 180 - for load = 0 output is 1010
# @time : 190 - for load = 0 output is 1011
# @time : 200 - for load = 0 output is 0000
# @time : 210 - for load = 0 output is 0001
# @time : 200 - for load = 0 output is 0000
# @time : 210 - for load = 0 output is 0001
# @time : 210 - for load = 0 output is 0001
# @time : 210 - for load = 0 output is 0001
# @time : 220 - for load = 0 output is 0010
# @time : 230 - for load = 0 output is 0011
# @time : 240 - for load = 0 output is 0100
# @time : 250 - for load = 0 output is 0101
# @time : 260 - for load = 0 output is 0110
# @time : 270 - for load = 0 output is 0111
# @time : 280 - for load = 0 output is 1000
# @time : 290 - for load = 0 output is 1001
# @time : 300 - for load = 0 output is 1010
# @time : 310 - for load = 0 output is 1011
# @time : 320 - for load = 0 output is 0000
# @time : 330 - for load = 0 output is 0001
# @time : 340 - for load = 0 output is 0010
# @time : 350 - for load = 0 output is 0011
# @time : 360 - for load = 0 output is 0100
# @time : 370 - for load = 0 output is 0101
# @time : 380 - for load = 0 output is 0110
# ** Note: $finish : C:/Users/Aadhithan/Documents,
/count_tb.v(24)
# Time: 385 ps Iteration: 0 Instance: /count_tb
# 1


```

RTL:

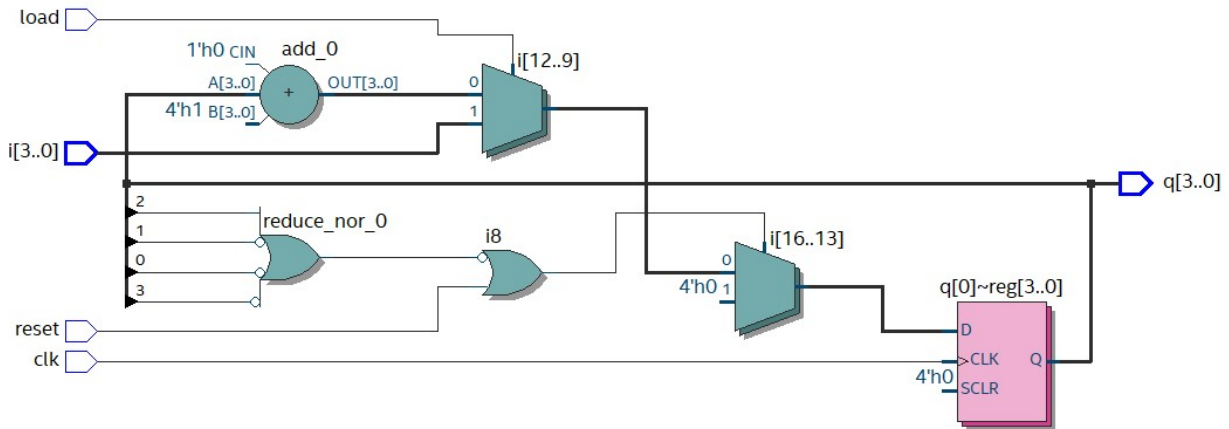

Design : up/down counter:

Wave:

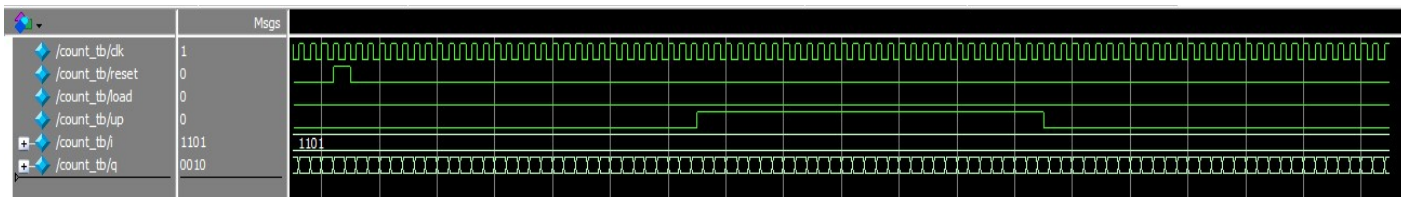

Output:

[illegible]

RTL:

